

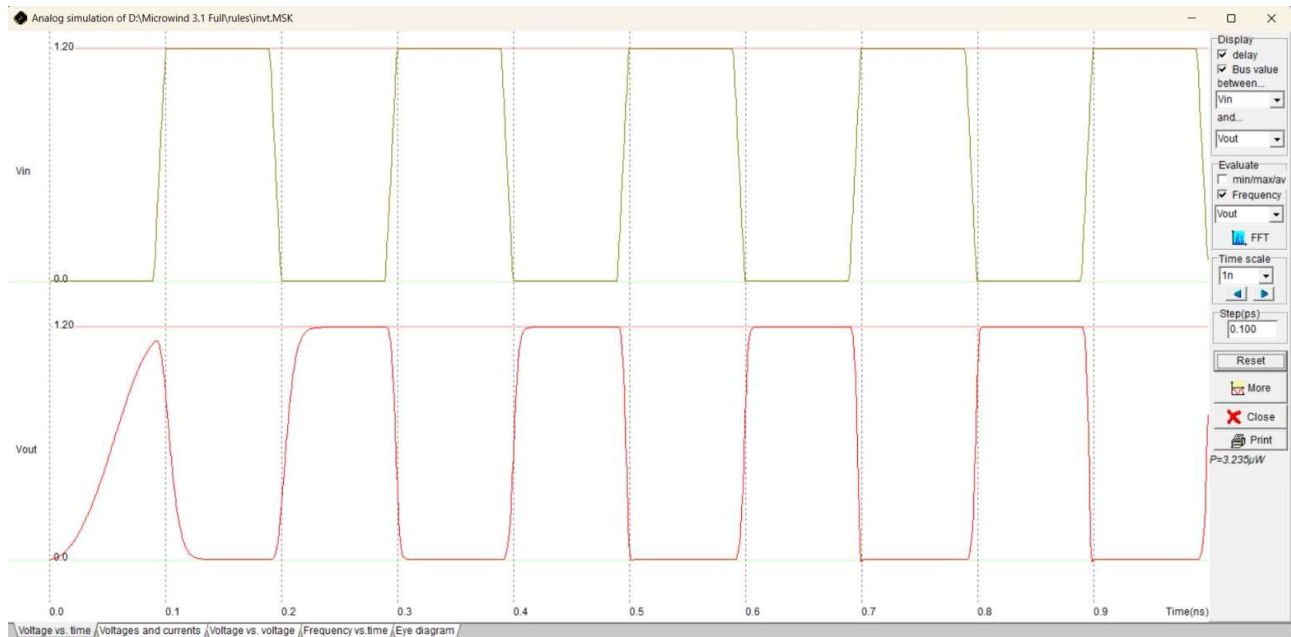
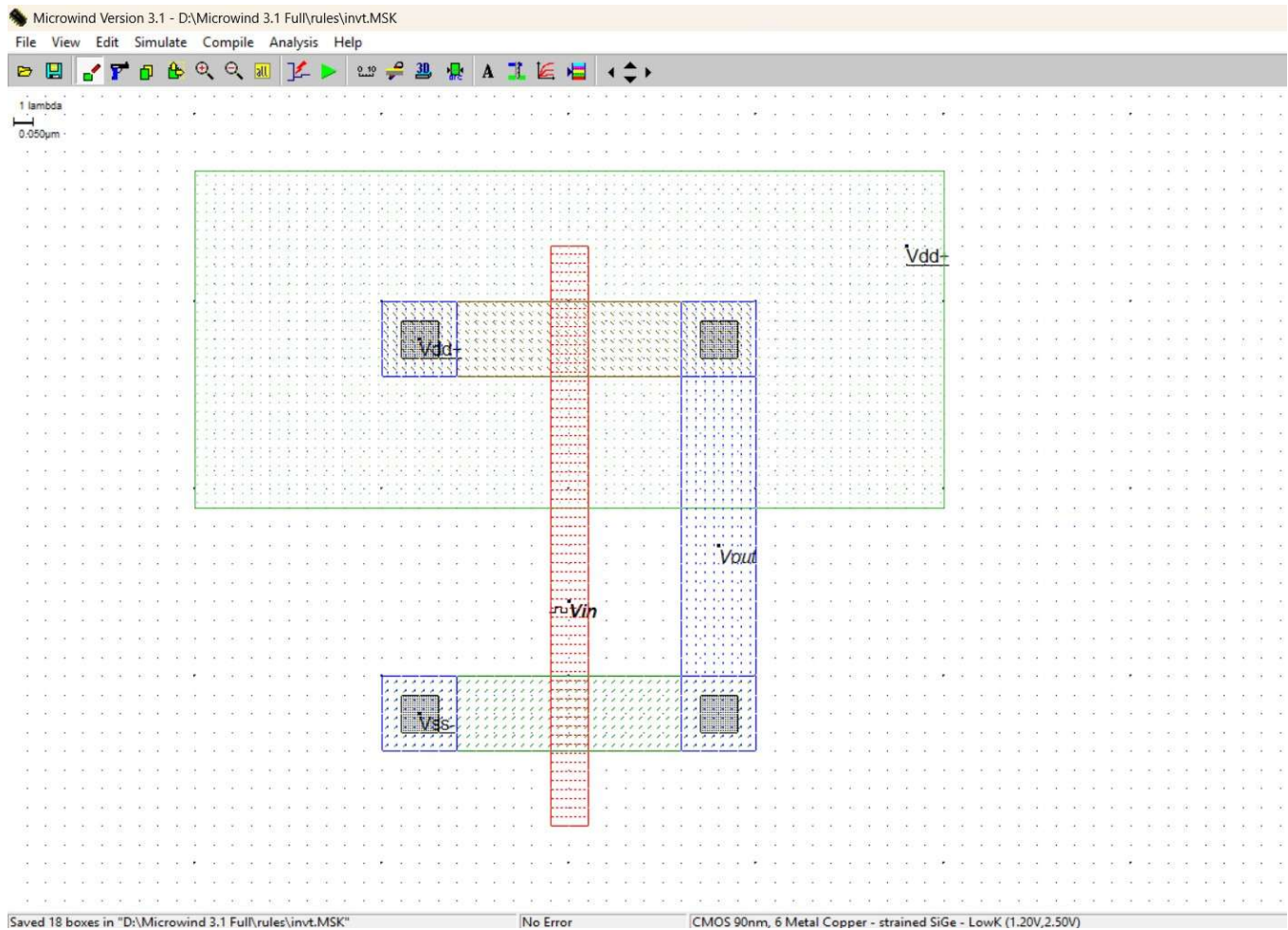



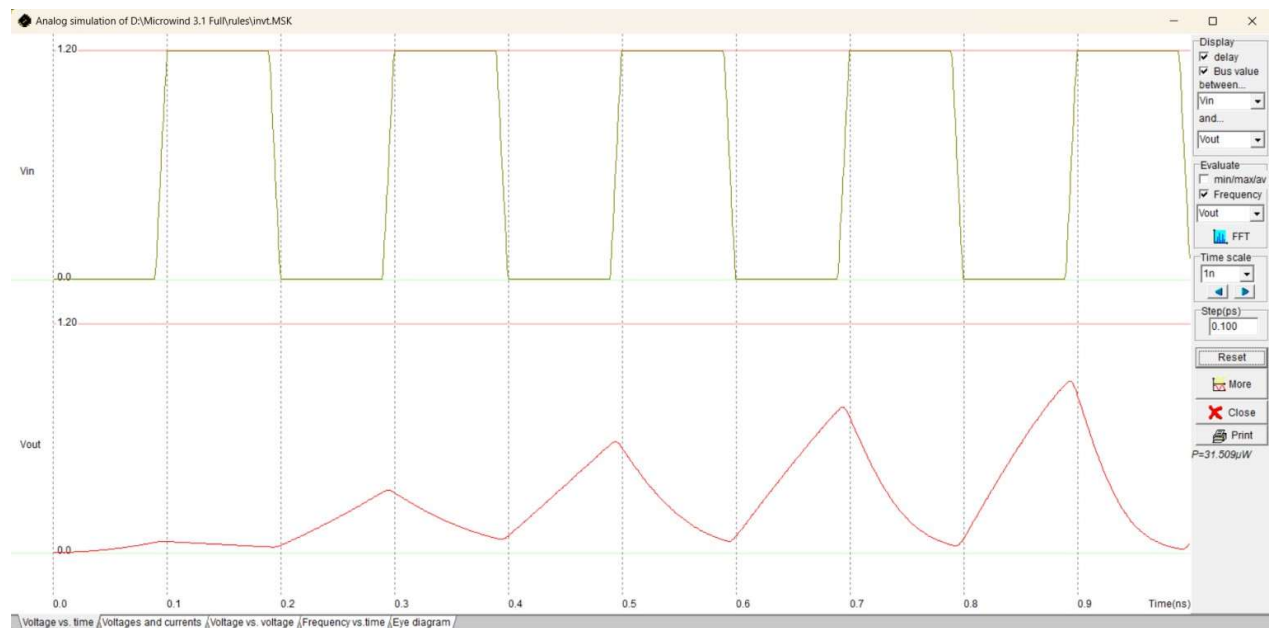
CMOS Inverter (symmetrical without capacitor)




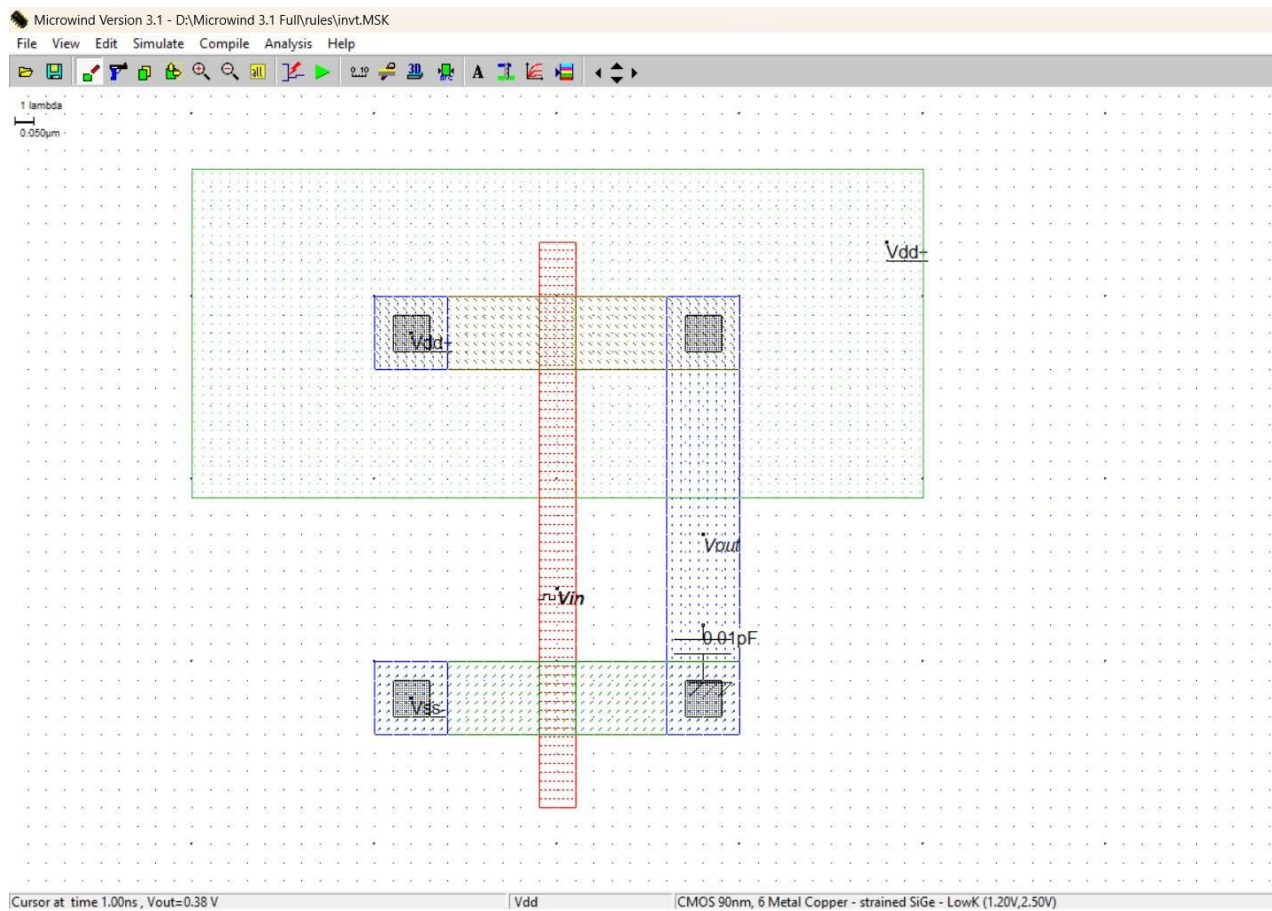
CMOS Inverter (symmetrical with capacitor)



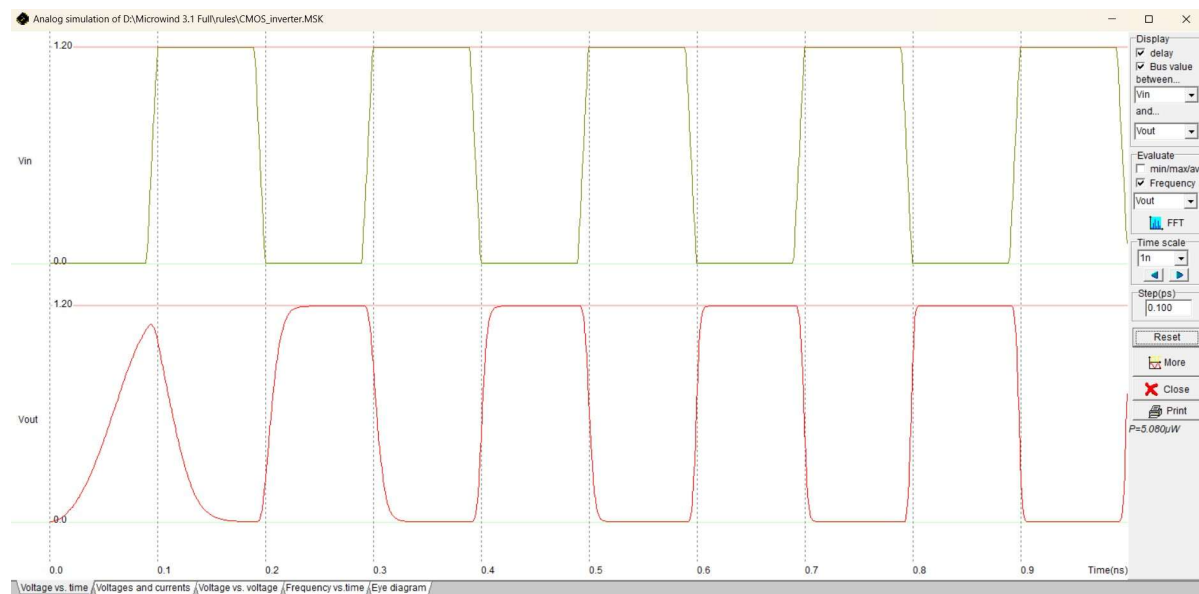
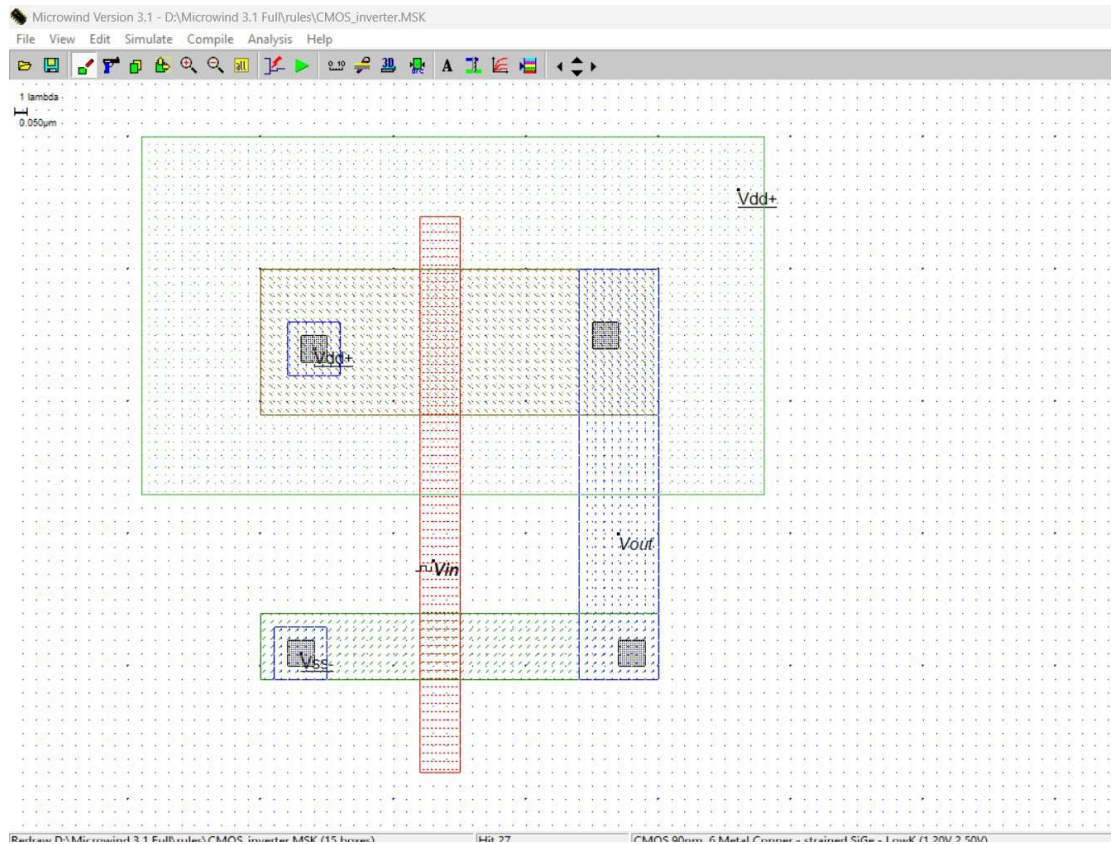
CMOS Inverter (Asymmetrical without capacitor)



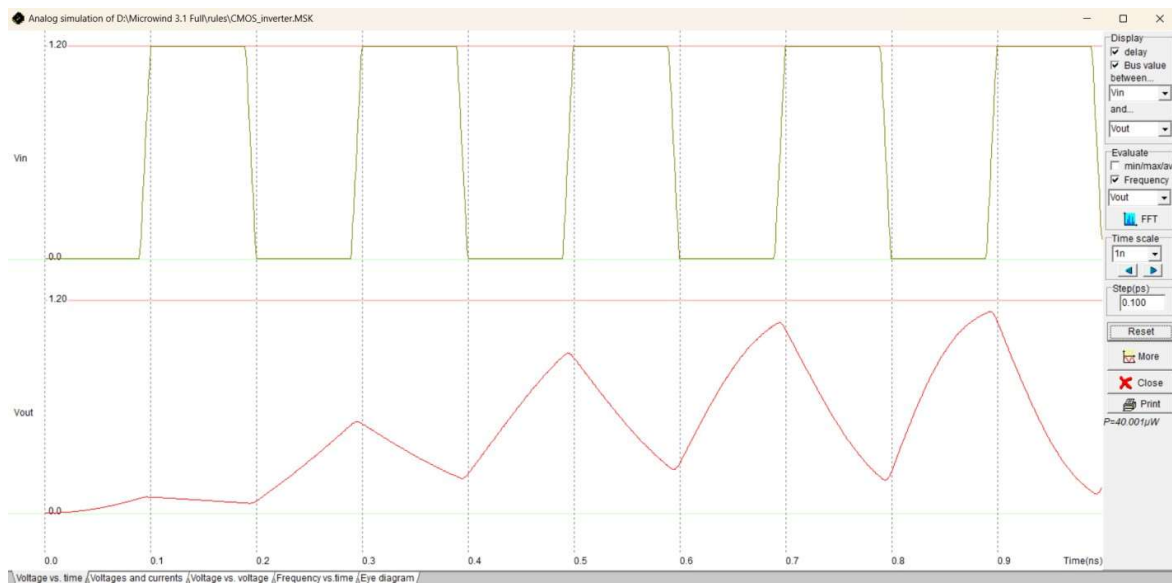
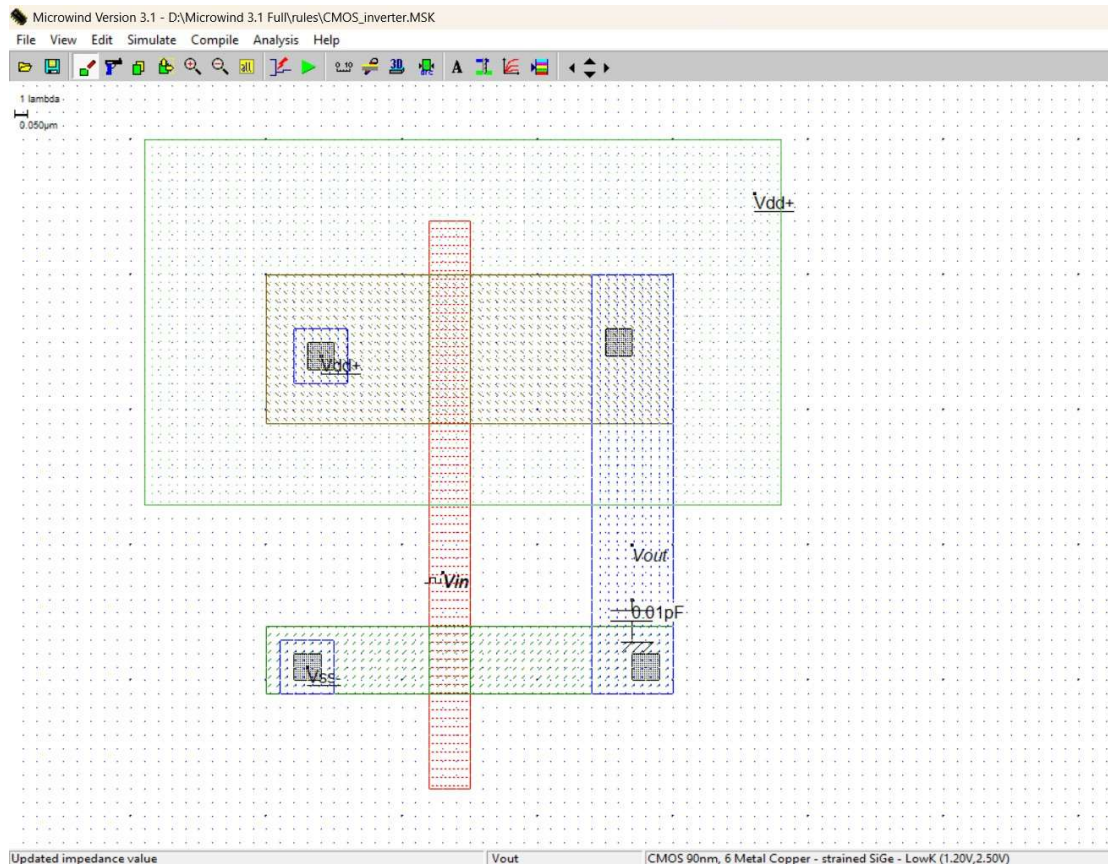
CMOS Inverter (Asymmetrical with capacitor)





NOR (without Capacitor)

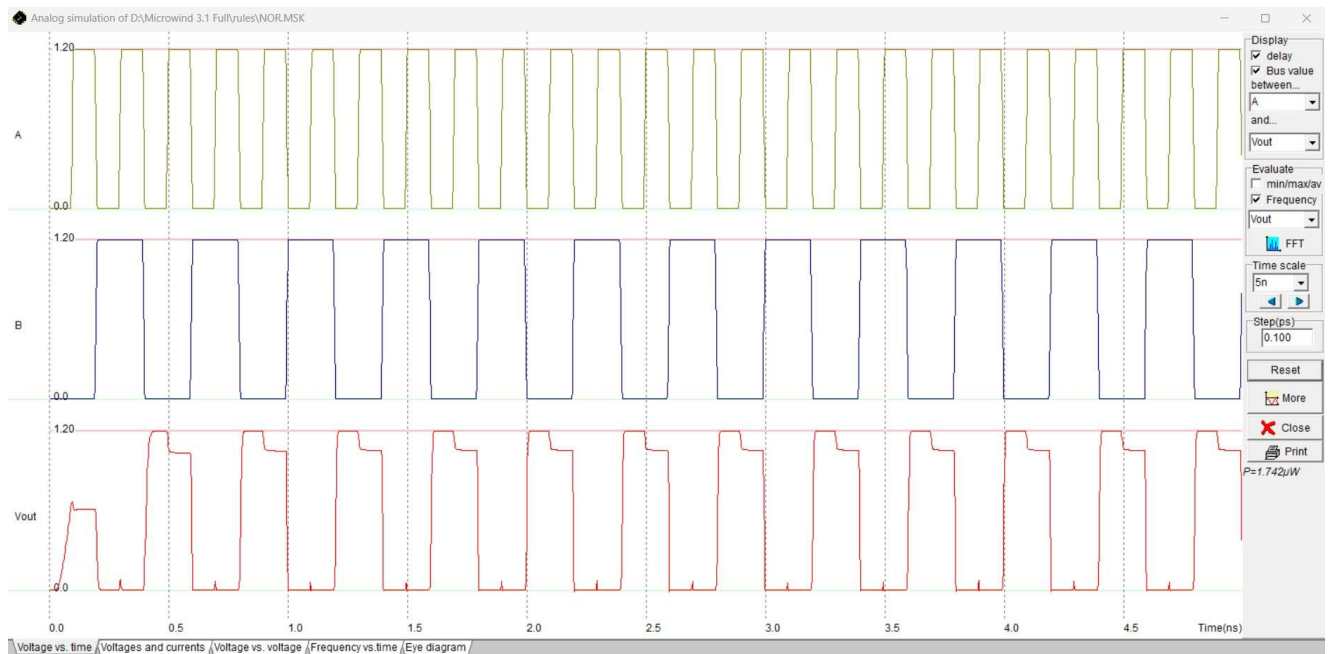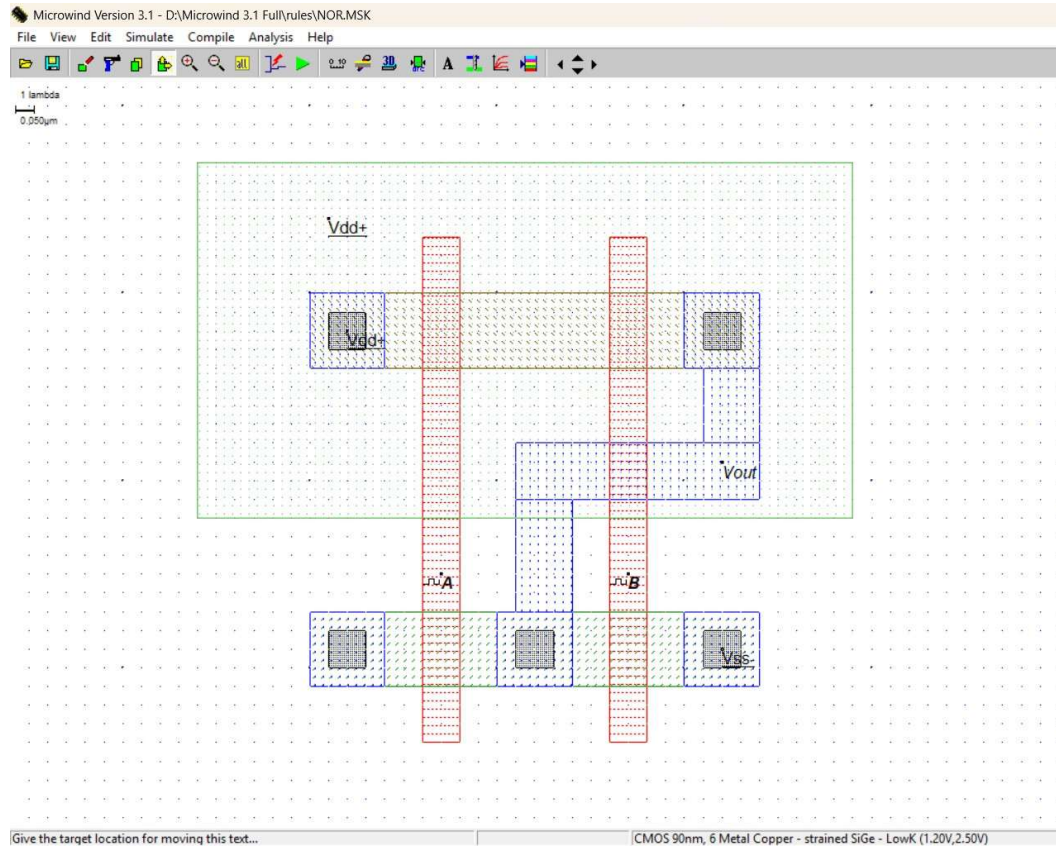



NOR (with capacitor)

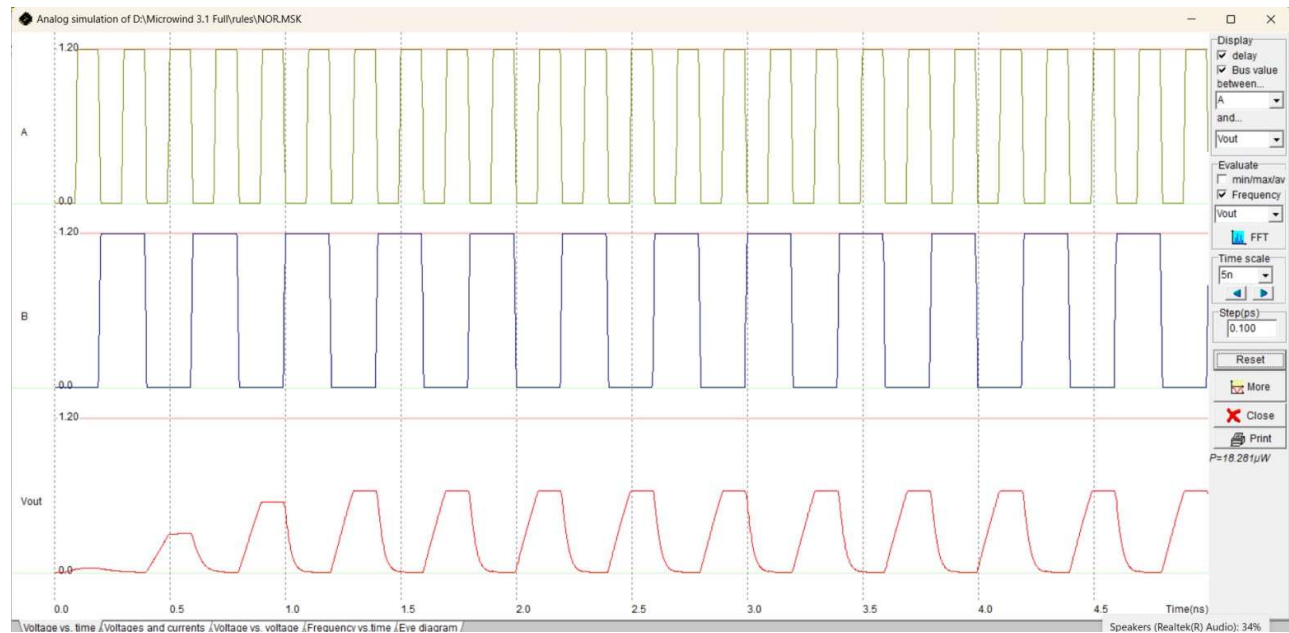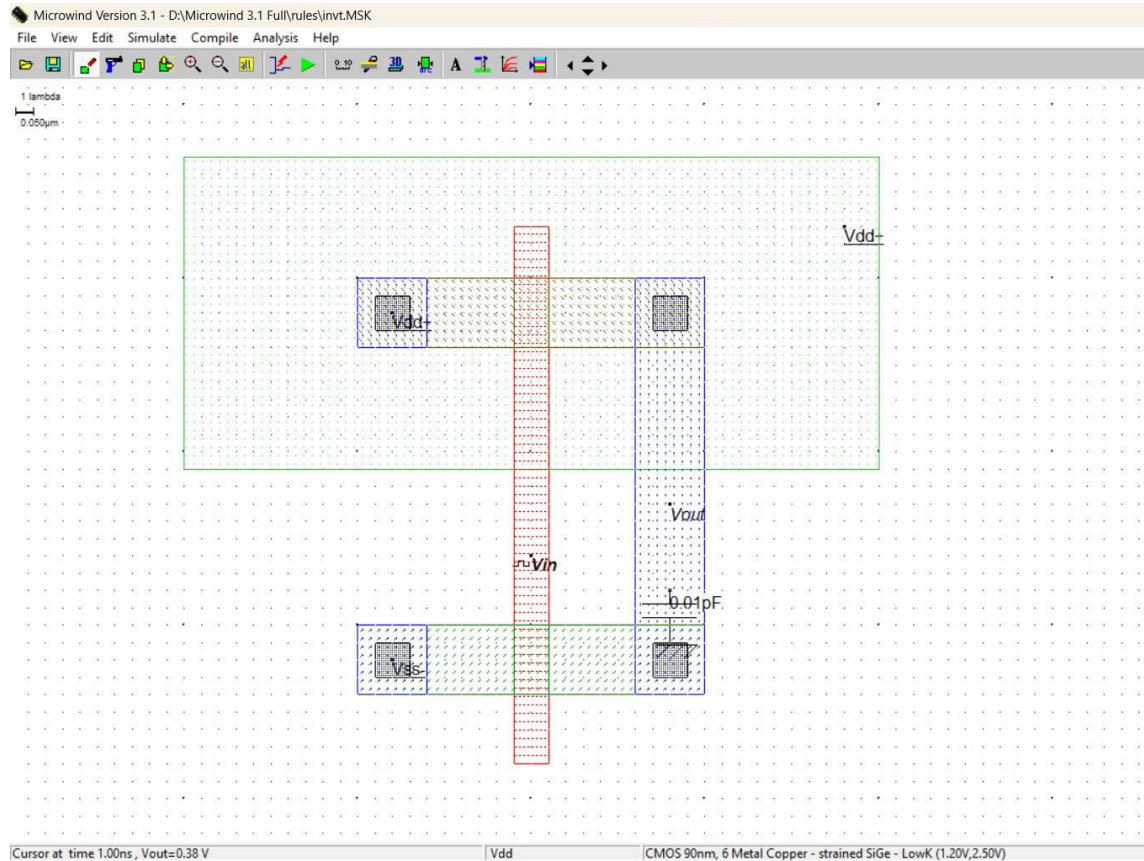

NAND (without capacitor)

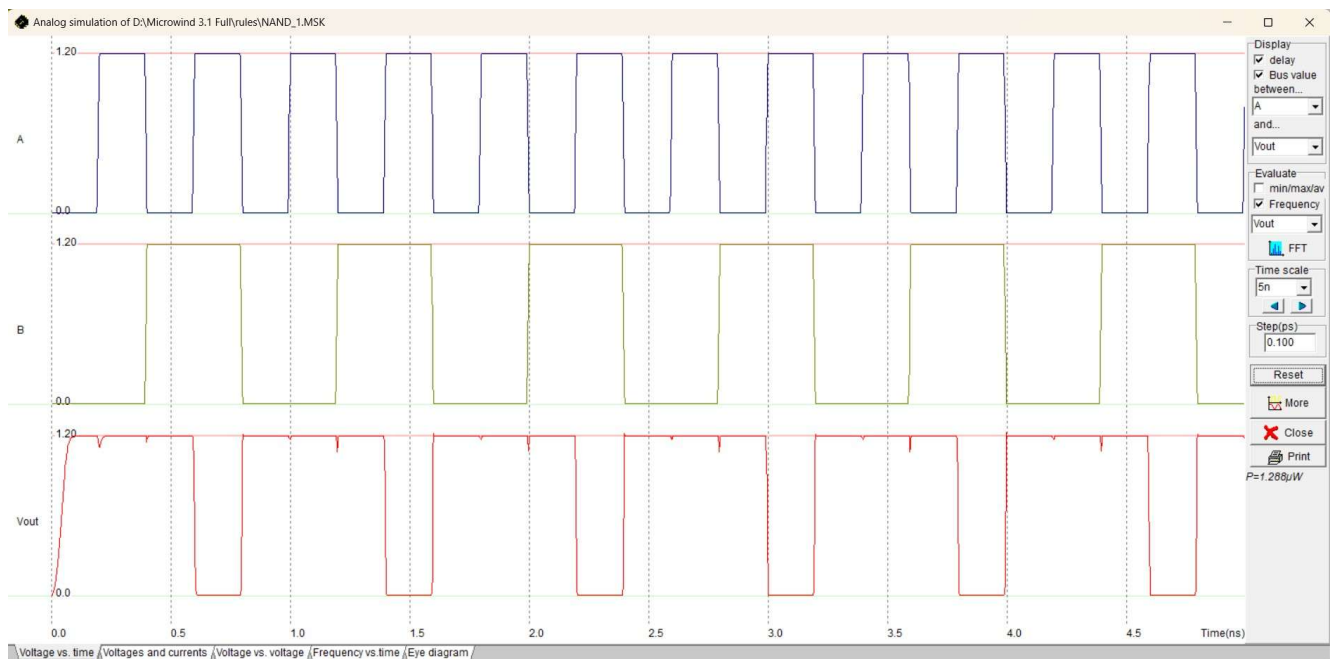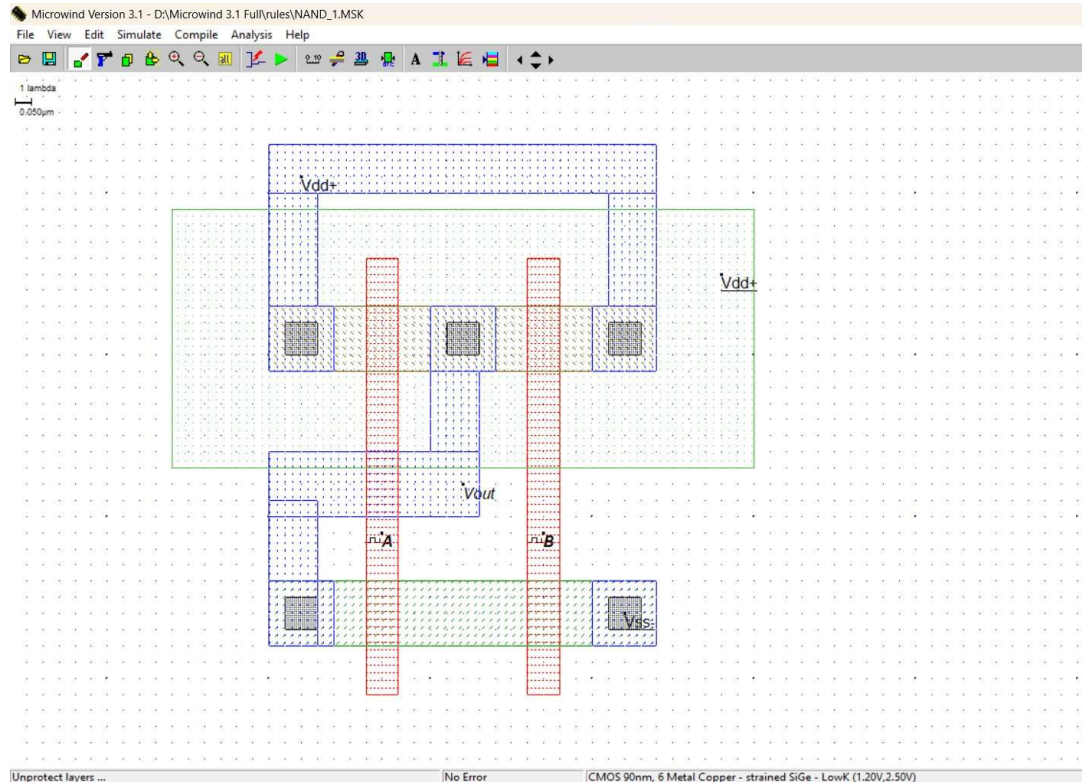

NAND (with capacitor)

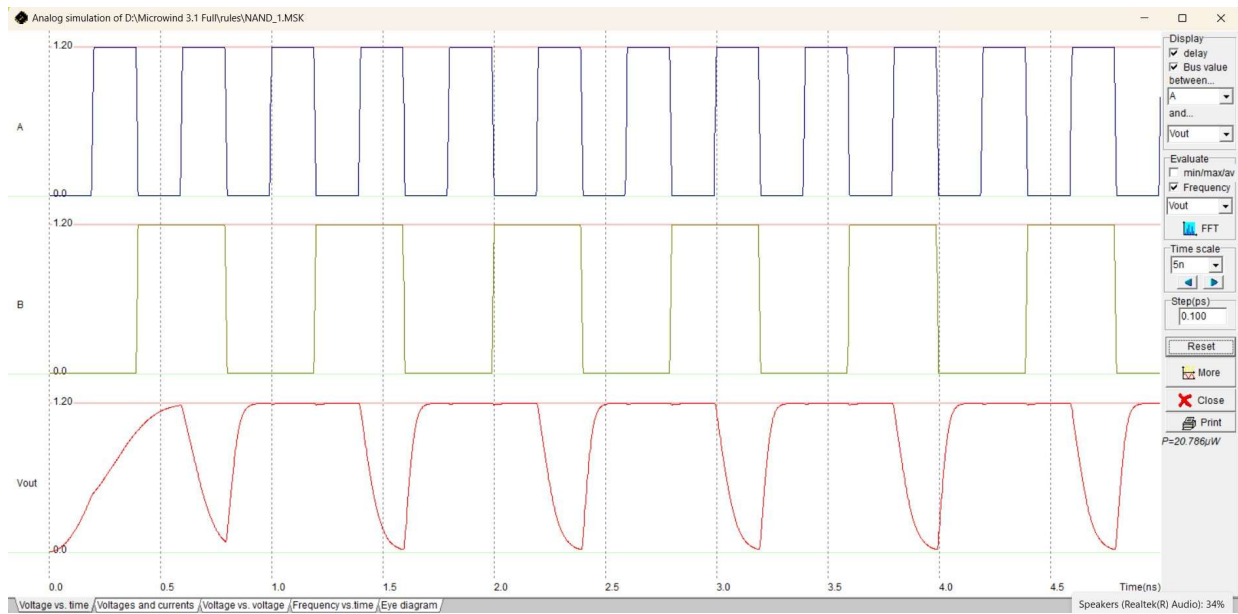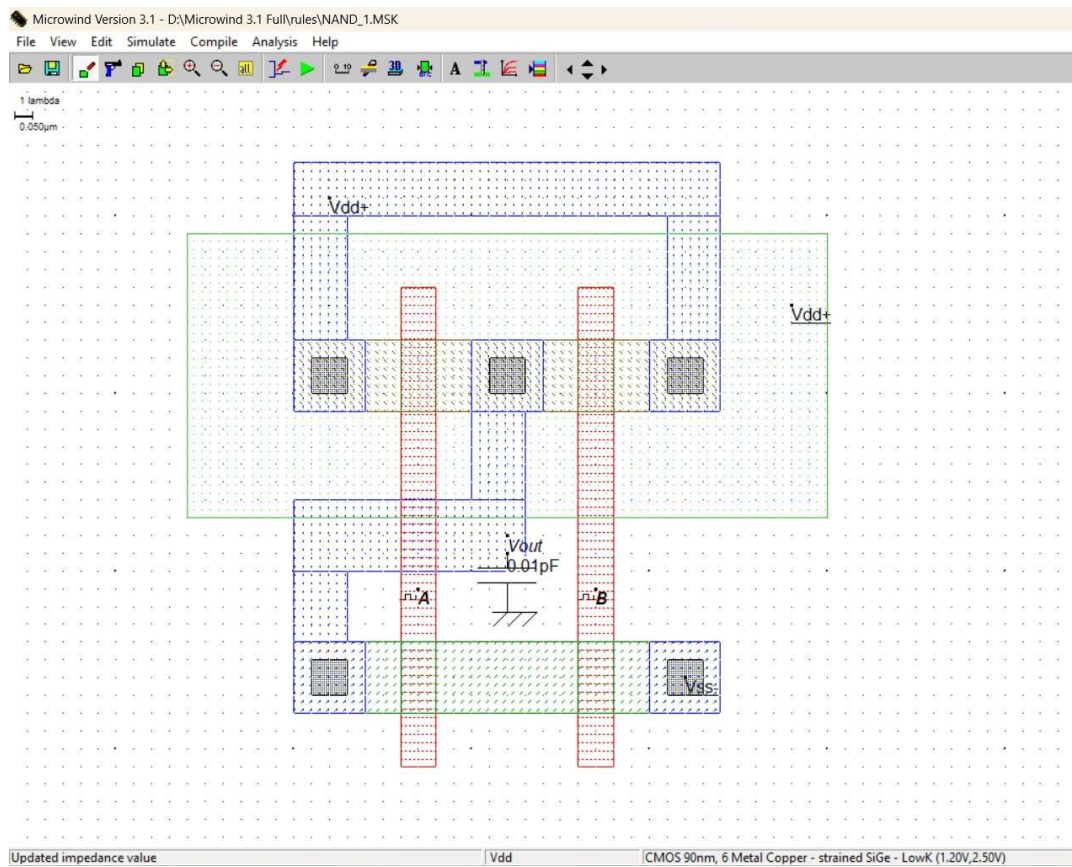

Half Adder

